

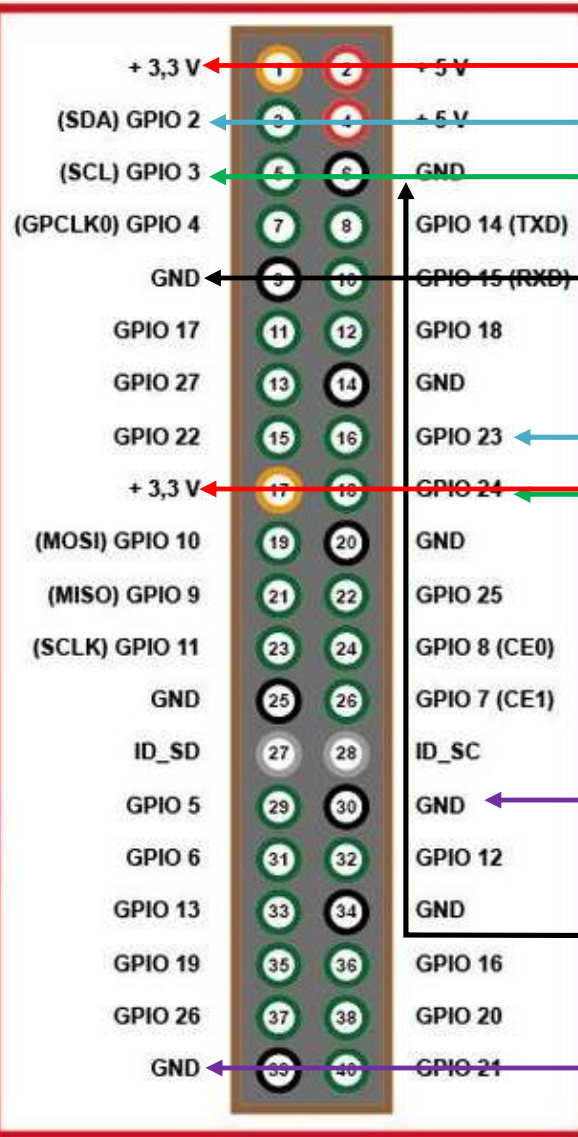




Wiring diagram light sensors

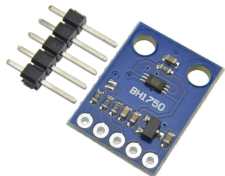


Top Sensor

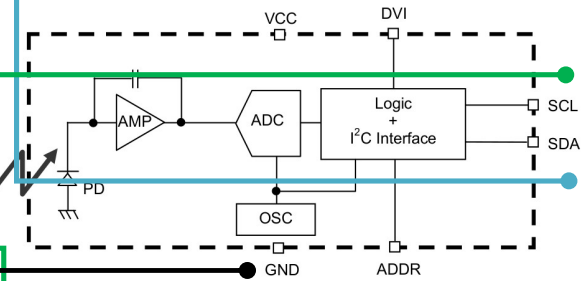

Bottom sensor

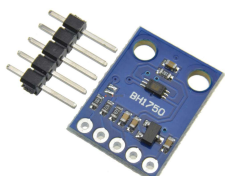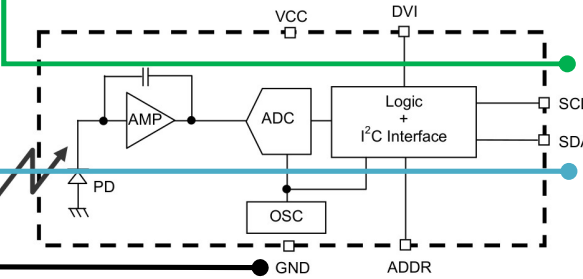

Wiring diagram servos

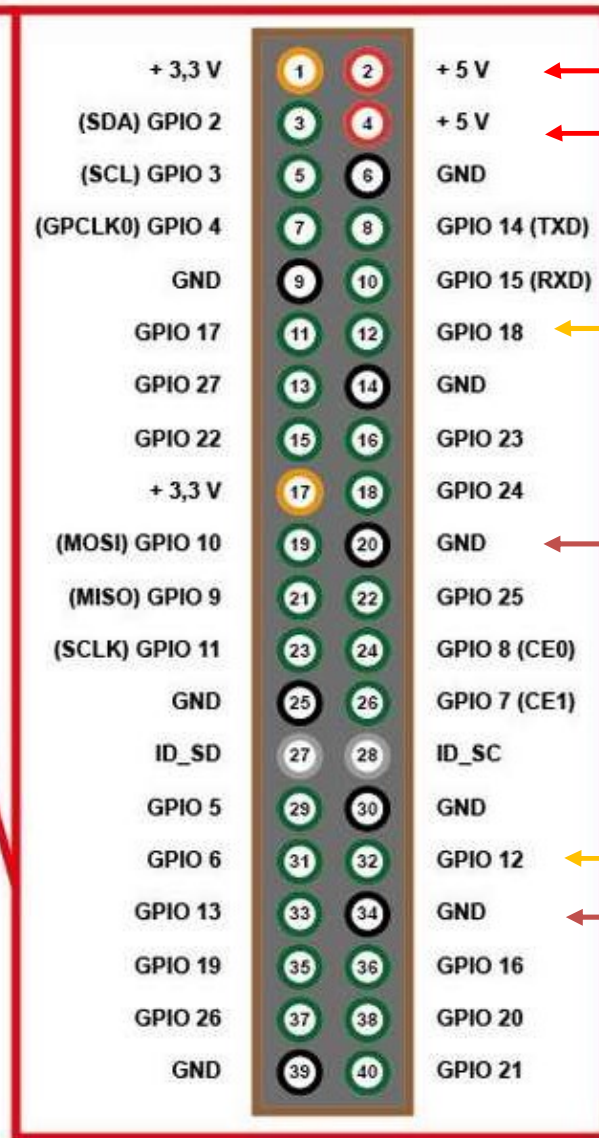

Servo on fork



Servo in housing

